Pg 1

Goal { To equip you with circuit analysis tools that are crucial for modern & future chips!

KCL + KVL — Lumped element

Pg 2

Topics

Circuits basics ⇐ Laplace domain

⇓

(L ⇔ C ⇔ Resist

Node & Mesh Analysis → Sym ⇒ Asymmetry


Network theorems


Two-port Networks

Freq & time domain analysis

Misc (power/high-voltage)


Example

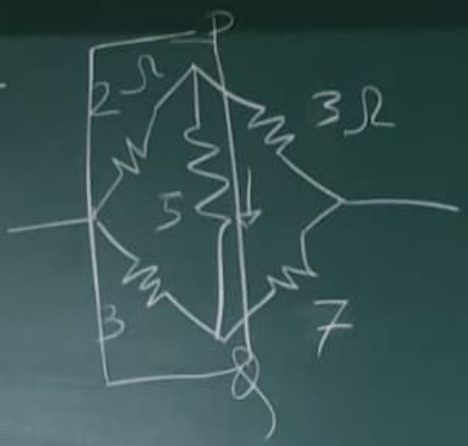

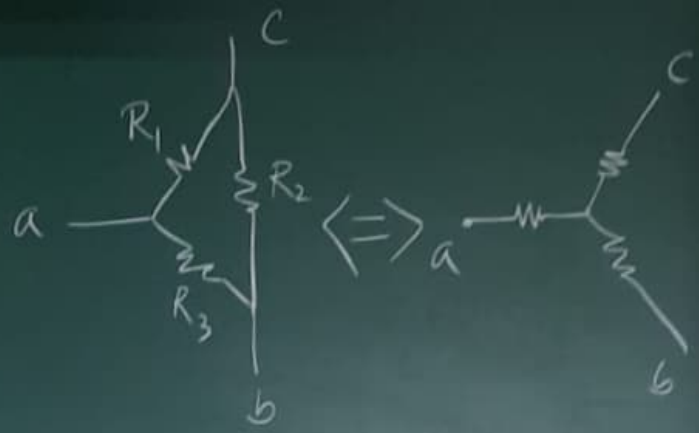


KCL/KVL

Example

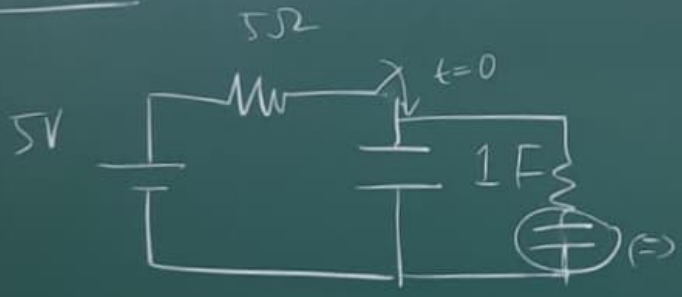

At what t, $V_c \geq 4.95V$?

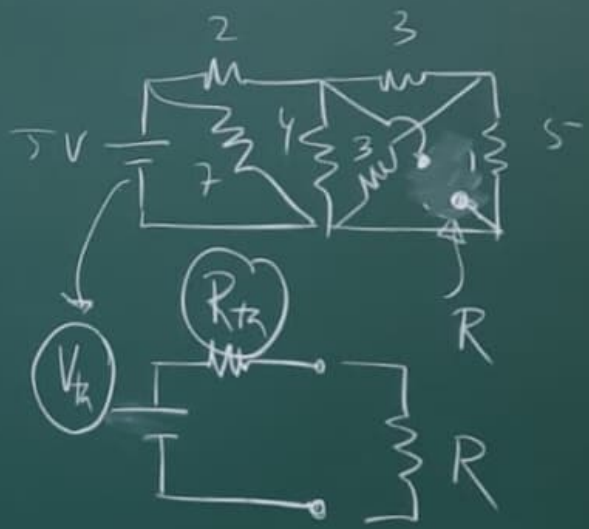

C slot

Mon 10 am
Tue 9 am
Wed 8 am
} Lectures

Fri 1 pm ← tutorial

Office hours: 11:30-12:30 Mon
ESB 323

Grading

Quiz I 20%
II 20%
Final 60%

Institute schedules

Textbook: Engg Circuit Analysis 9th ed
Hayt & Kemmerly (Dublon!)