

EE2015: Electric Circuits and Networks

Tutorial 4


(September 12, 2025)

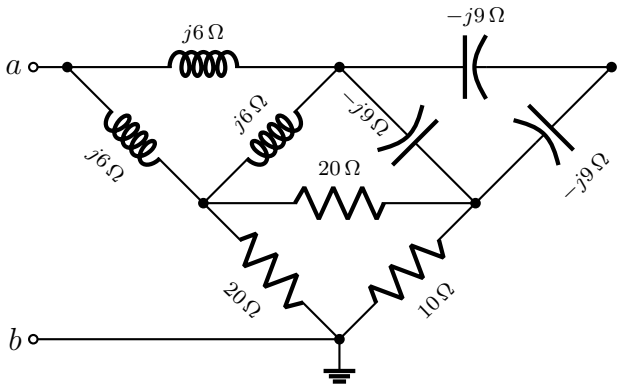
1. Calculate the impedance $\mathbf{Z}_{ab}$ of the one-port networks shown below.



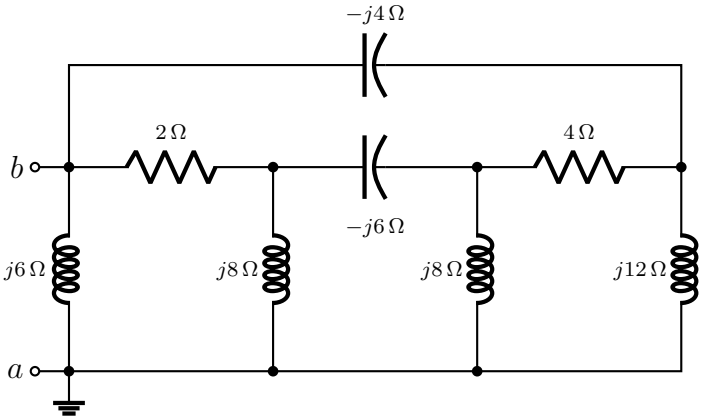


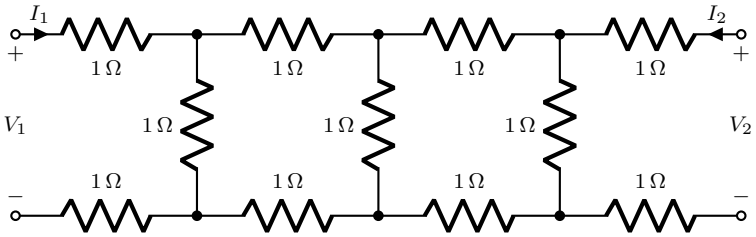2. For the two-port network shown on the right find the impedance and admittance parameters.



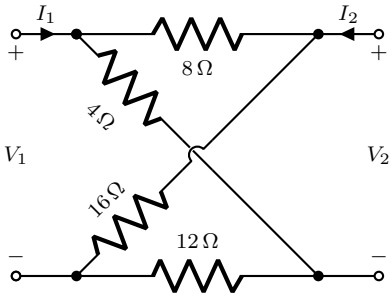3. 

Determine the z- and y-parameters of the two-port network shown on the left.

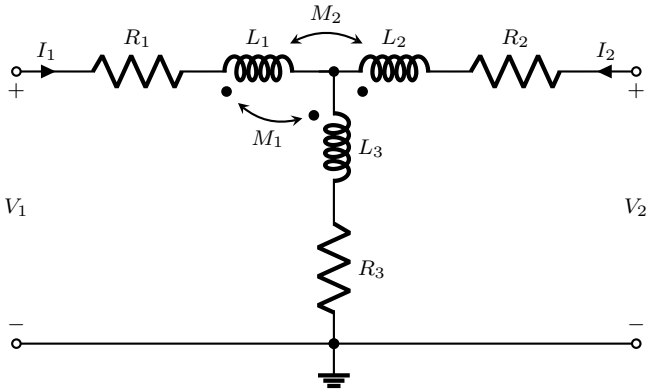4. 

Find the entries of $\mathbf{Z}(s)$ of the two-port network shown on the right.

5. Find the z-parameters for the two-port network shown on the right.

