
EE2015: Electric Circuits and Networks

Tutorial 5


(September 19, 2025)

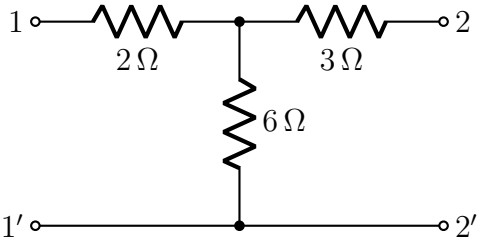1.

Find the h-parameters of the circuit shown on the right.




2.

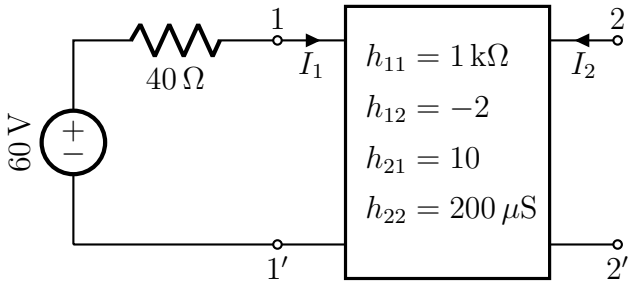


The h-parameters of a two-port network are as shown on the left. Find the Thevenin equivalent as seen at the output terminal pair $22'$.

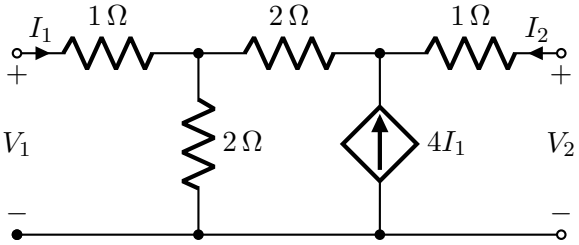3.

Find the h-parameters of the two-port network shown on the right.




4.

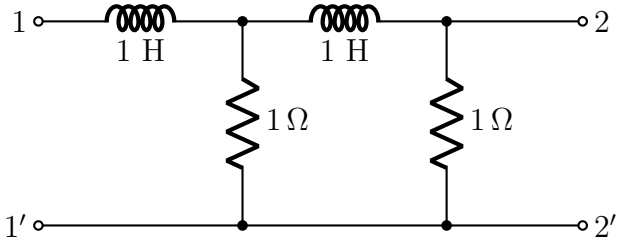


Find the ladder network shown on the left, determine the g-parameters in the s-domain.

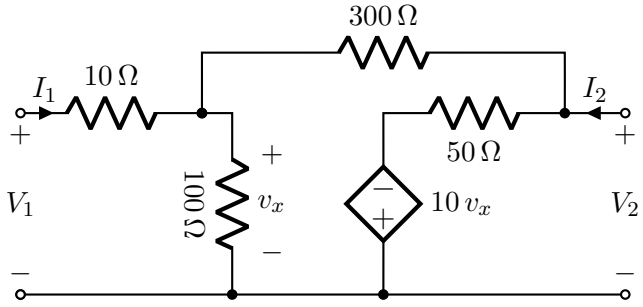5.

Determine the h- and g-parameters of the two-port network shown on the right



6.

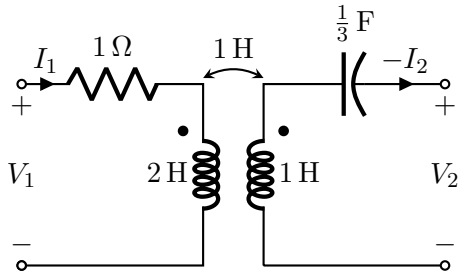

Find the *abcd* parameters of the two-port network shown on the left.

7. The T-parameters of a network are as shown below. The output port is connected to a variable resistor R_L and adjusted for maximum power transfer. Find R_L and the value of the maximum power transferred.

